



---

# **DLD Lab-12**

## **FlipFlops**

---



**Instructor: Mazhar Iqbal**

**EL227 – Digital Logic Design-Lab**

**SEMESTER SPRING 2021**

## Contents

1. Objectives: .....	2
2. Equipment Required: .....	2
3. Description: .....	2
Flip Flops .....	2
4. JK- FLIP FLOP .....	3
5. T- FLIP FLOP .....	4

## 1. Objectives:

- Getting familiar with characteristic tables and characteristic functions of flip-flops
- Gaining a close insight into the functioning and properties of basic static memory circuits
- Developing skills in the composition and testing of sequential logic circuits

## 2. Equipment Required:


- DEV-2765E Trainer Board/ Multisim 14.2 /Logic.ly
- 7486 XOR Gate IC
- 7408 AND Gate IC
- 7432 OR Gate IC
- 7404 Inverter Gate IC
- 7474 Dual +ve edge triggered D-Flip Flop
- 74112 Dual –ve edge triggered JK-Flip Flop

## 3. Description:


### Flip Flops

A flip-flop is usually constructed by combining two same or different types of latches. Flip-flop circuits are constructed in such a way as to make them operate properly when they are a part of a sequential circuit that employs a single clock. Note that the problem with the latch is that as soon as an input changes, shortly thereafter the corresponding output changes to match it. This is what allows a change on a latch output to produce additional changes at other latch outputs while the clock pulse is at logic 1. The key to the proper operation of flip-flops is to prevent them from being transparent. In a flip-flop, before an output can change, the path from its inputs to its outputs is broken. So a flip-flop cannot “see” the change of its output or of the outputs of other, like flip-flops at its input during the same clock pulse. Thus, the new state of a flip-flop depends only on the immediately preceding state, and the flip-flops do not go through multiple changes of state. The edge triggered D flip flop avoids the problem of the RS invalid output states by not allowing the invalid states. The JK flip flop is a clocked RS flip flop with additional logic to replace the RS invalid output states with a new mode called toggle. Toggle causes the flip flop to change to the state opposite to its present state.

## 4. JK- FLIP FLOP

 


Positive Edge Triggered

 

Negative Edge Triggered

### Positive Edge Triggered JK Flip Flop

 
#### Circuit Diagram using D-flip Flop and basic gates




#### Characteristic Table for JK Flip Flop:

Inputs		Outputs		Next State of Q
J	K	Q	$\sim Q$	
0	0			
0	1			
1	0			
1	1			

## 5. T- FLIP FLOP

 

Positive Edge Triggered

 

Negative Edge Triggered

### **Positive Edge Triggered T-Flip Flop**

#### **Circuit Diagram using D-flip Flop and basic gates**




#### **Characteristic Table for T Flip Flop:**

T	Output
0	
1	

### **Negative Edge Triggered JK Flip Flop**
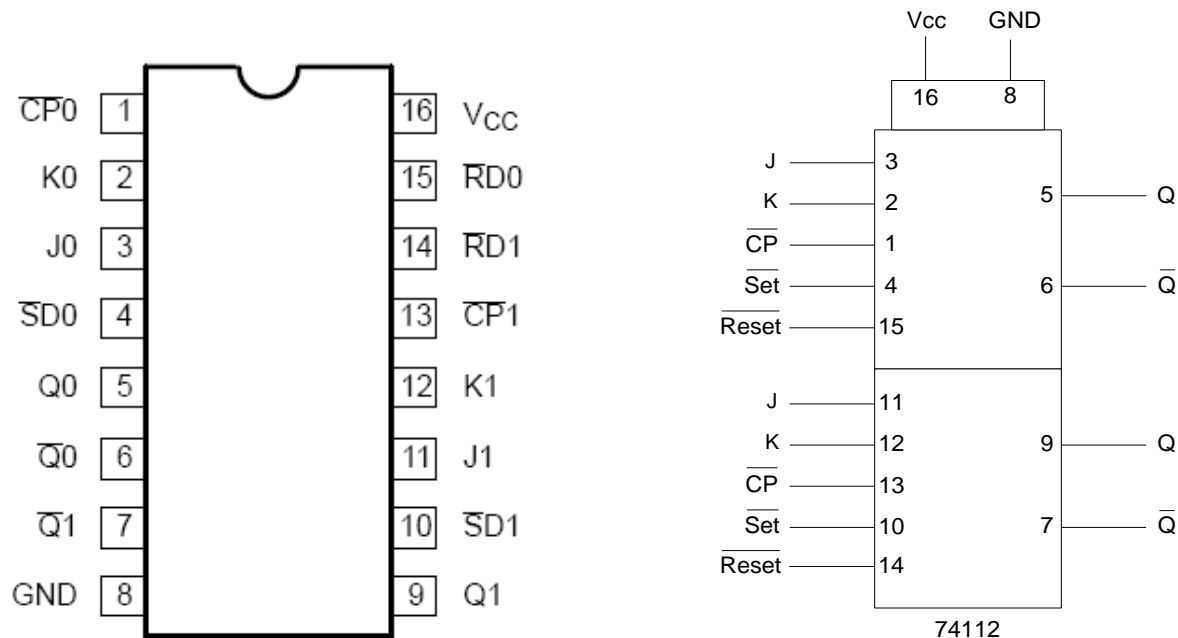
#### **Pin Configuration of 74112 (JK-FFP):**



### Description of PINS:

The 74F112, Dual Negative Edge-Triggered JK-Type Flip-Flop, feature individual J, K, Clock (CPn), Set (SD) and Reset (RD) inputs, true (Qn) and complementary ( $\sim$ Qn) outputs. The SD and RD inputs, when Low, set or reset the outputs as shown in the Function Table, regardless of the level at the other inputs. A High level on the clock (CPn) input enables the J and K inputs and data will be accepted. The logic levels at the J and K inputs may be allowed to change while the CPn is High and flip-flop will perform according to the Function Table as long as minimum setup and hold times are observed. Output changes are initiated by the High-to-Low transition of the CPn.

### Function Table:

INPUTS					OUTPUTS		OPERATING MODE
SD	RD	CP	J	K	Q	Q	
0	1	X	X	X	1	0	Asynchronous Set
1	0	X	X	X	0	1	Asynchronous Reset
0	0	X	X	X	1*	1*	Undetermined *
1	1	↓	1	1	$\sim$ q	q	Toggle
1	1	↓	0	1	0	1	Load "0" (Reset)
1	1	↓	1	0	1	0	Load "1" (Set)
1	1	↓	0	0	q	q	Hold "no change"
1	1	1	X	X	Q	Q	Hold "no change"

\* = Both outputs will be High while both SD and RD are Low, but the output states are unpredictable if SD and RD go High simultaneously

### Procedure

1. Connect the trainer with the power supply

2. Mount the IC 74LS112 on the trainer board
3. Supply the VCC and GND to the pin 16 and 8 respectively
4. Connect only one of the two flip-flops available on the IC. Refer to the pin configuration and characteristic table (function table) for this IC is given above.
5. Drive the J, K and CK inputs input switch on the trainer board and CP input from the clock on the trainer board. Connect output  $Q_0$  &  $\sim Q_0$  with the LED.
6. Be sure to connect the set (SD) and reset (RD) inputs to a logical 1.
7. Using the different input combinations, verify the JK flip-flop characteristic table.
8. Observe and record the output on the LED.

**Tasks:**

- a) Implement JK-Flip Flop using D-flip Flop IC and basic Gates on Trainer Board and verify its truth table.
- b) Modify part (a) to implement T-Flip Flop.
- c) Verify JK-Flip Flop truth table using 74LS112 IC.
- d) Modify part (c) to design a T-Flip Flop.