



DLD Lab-09

Multiplexer & De Multiplexer



Instructor: Mazhar Iqbal

EL227 – Digital Logic Design-Lab

SEMESTER SPRING 2021

FEBRUARY 9, 2022

NATIONAL UNIVERSITY OF COMPUTER AND EMERGING SCIENCES, FAST- PESHAWAR CAMPUS
Department Of Computer Science

Contents

1. Objectives:	2
2. Equipment Required:	2
3. Background Theory	2
4. 4x1 Mux Contd.....	3
5. 4x1 Mux(74LS153 Testing in Multisim).....	4
6. 8x1 Mux.....	4
7. 8x1 Mux(74LS151 Testing in Multisim).....	5
8. DE Multiplexer	6
9. 1x4 De Multiplexer.....	6
10. 1x4 De-Mux(74LS139 Testing in Multisim).....	7
11. 1x8 De Multiplexer	8

1. Objectives:

- Design and implement the circuitry for a 4 to 1 Multiplexer.
- Test the functionality of a 1x4 DE multiplexer using the IC-74LS139
- Test the functionality of a 8x1 multiplexer using the IC-74LS151
- Test the functionality of a 4x1 multiplexer using the IC-74LS153 Gaining a close insight into the functioning and properties of multiplexer (MUX) circuits
- Developing skills in the design and testing of combinational logic circuits.

2. Equipment Required:

- DEV-2765E Trainer Board/ Multisim 14.2 /Logic.ly
- 74LS04 Hex Inverter
- 74LS08 And gate
- 74LS32 OR gate
- 74LS151 (8-to-1 Multiplexer)
- 74LS153 (dual 4-to-1 Multiplexer)

3. Background Theory

A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs the information to a single output line. The selection of a particular input line is controlled by a set of input variables, called selection input. Normally, there are 2^n input lines and n selection inputs whose bit combination determines which input is selected.

A demultiplexer is doing the opposite function of multiplexer. It takes input on a single input line and the select lines determine one of the 2^n output lines and the input contents is visible on that particular output.

The multiplexer is a device that has **multiple inputs** and **single line output**. The **select lines** determine which input is connected to the output in other words

Multiplexer is a combinational circuit that has maximum of 2^n data inputs, ' n ' selection lines and single output line.

Multiplexer is also called as **Mux**.


 


Figure 1

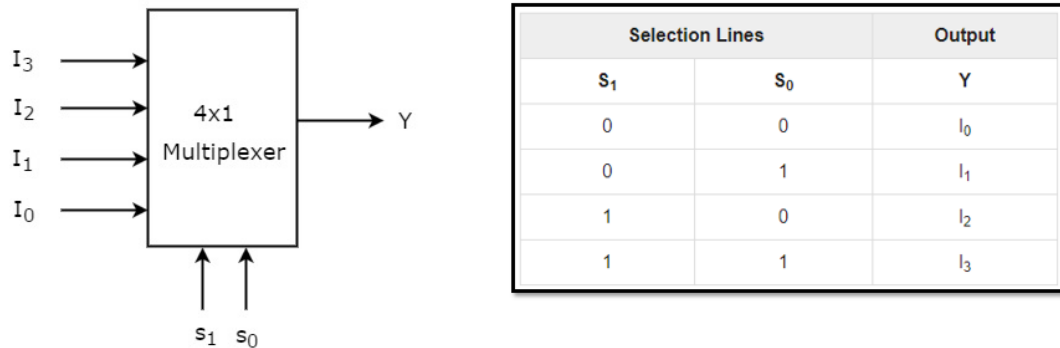
4. 4x1 Mux Contd.

4x1 Multiplexer has four data inputs I_3, I_2, I_1 & I_0 , two selection lines s_1 & s_0 and one output Y . The **block diagram** of 4x1 Multiplexer is shown in the following figure.




$$Y = s_1's_0'I_0 + s_1's_0I_1 + s_1s_0'I_2 + s_1s_0I_3$$

 
We can implement this Boolean function using Inverters, AND gates & OR gate. The **circuit diagram** of 4x1 multiplexer is shown in the following figure.




5. 4x1 Mux(74LS153 Testing in Multisim)

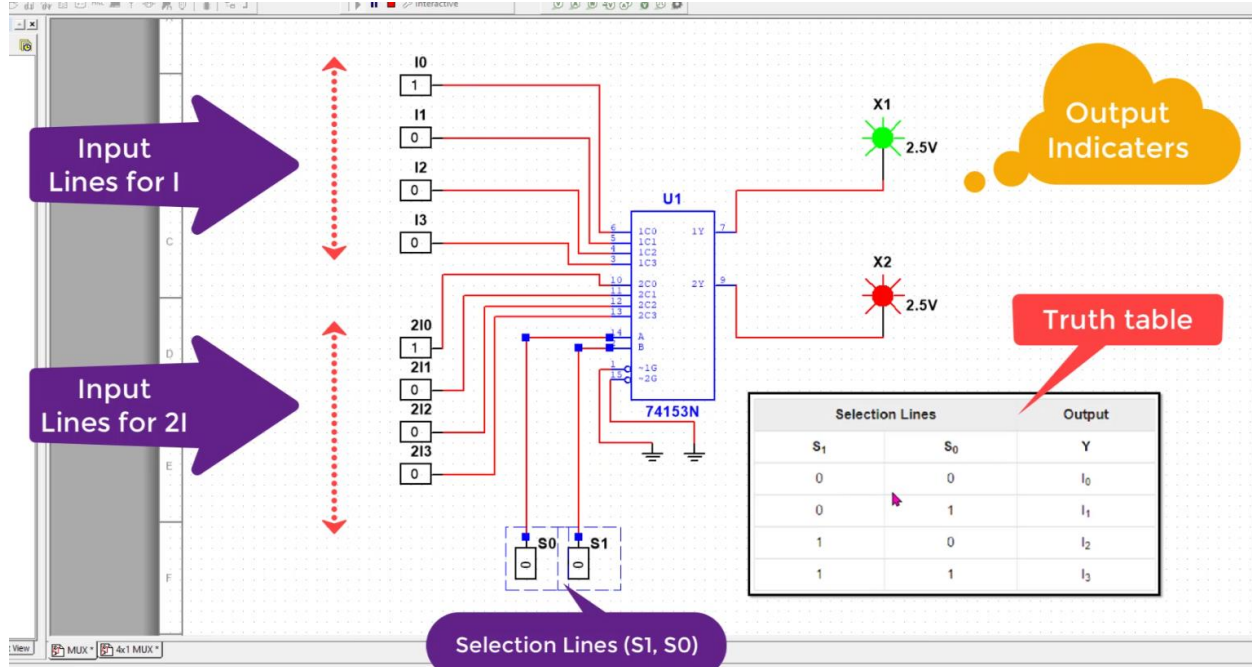


6. 8x1 Mux

 


Selection Inputs			Output
S ₂	S ₁	S ₀	Y
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇

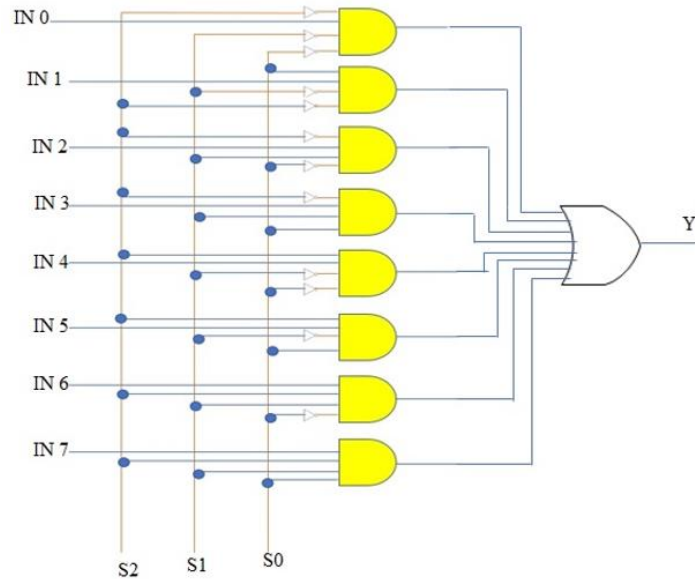
 
$$Y = S_2' S_2' S_0' I_0 + S_2' S_1' S_0' I_1 + S_2' S_1 S_0' I_2 + S_2' S_1 S_0 I_3 + S_2 S_1' S_0' I_4 + S_2 S_1' S_0 I_5 + S_2 S_1 S_0' I_6 + S_2 S_1 S_0 I_7$$




7. 8x1 Mux(74LS151 Testing in Multisim)

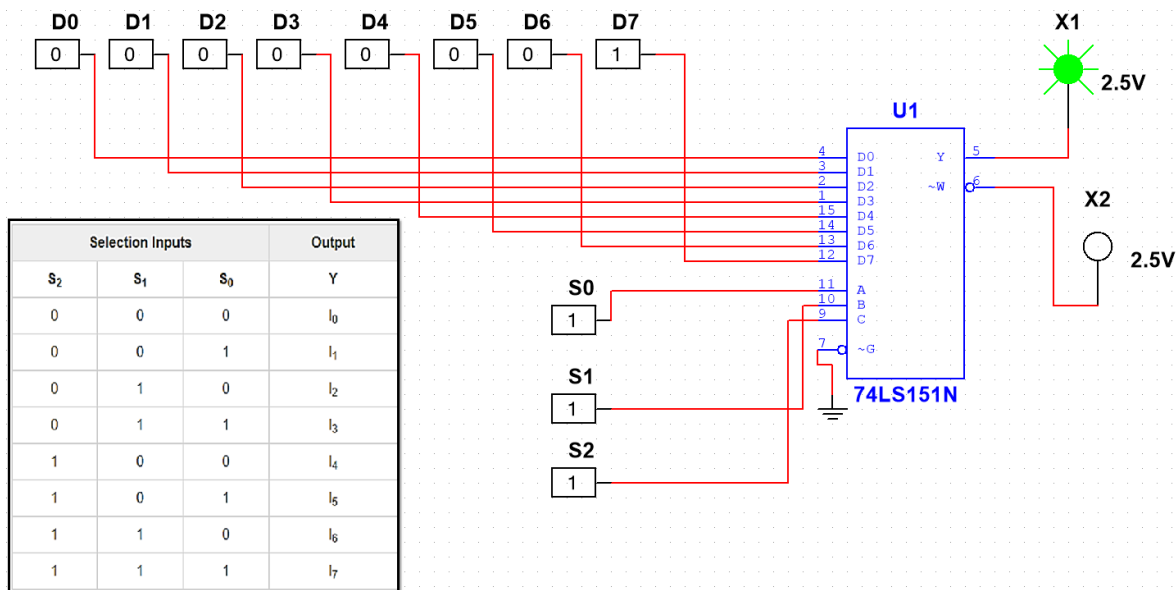

 
8. DE Multiplexer

The function of De multiplexer is in contrast to multiplexer function. It takes information from one line and distributes it to a given number of output lines. For this reason, the demultiplexer is also known as a data distributor. It has single input, 'n' selection lines and maximum of 2^n outputs. The input will be connected to one of these outputs based on the values of selection lines.



 9. 1x4 De Multiplexer

1x4 De-Multiplexer has one input I, two selection lines, s_1 & s_0 and four outputs Y_3, Y_2, Y_1 & Y_0 . The **block diagram** of 1x4 De-Multiplexer is shown in the following figure.





From the Truth table, we can directly write the **Boolean functions** for each output as

$$Y_3 = s_1 s_0 I$$


$$Y_2 = s_1 s_0 \bar{I}$$

$$Y_1 = s_1 \bar{s}_0 I$$

$$Y_0 = s_1 \bar{s}_0 \bar{I}$$

  

 
10. 1x4 De-Mux(74LS139 Testing in Multisim)



Selection Inputs		Outputs			
s_1	s_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	I
0	1	0	0	I	0
1	0	0	I	0	0
1	1	I	0	0	0

 11. 1x8 De Multiplexer

1x8 De-Multiplexer has one input I, three selection lines, s_2 , s_1 & s_0 and seven outputs Y_7 , Y_6 , Y_5 , Y_4 , Y_3 , Y_2 , Y_1 & Y_0 . The **block diagram** of 1x8 De-Multiplexer is shown in the following figure.



Selection Inputs			Outputs							
s_2	s_1	s_0	Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0	0	0	I
0	0	1	0	0	0	0	0	0	I	0
0	1	0	0	0	0	0	0	I	0	0
0	1	1	0	0	0	0	I	0	0	0
1	0	0	0	0	0	I	0	0	0	0
1	0	1	0	0	I	0	0	0	0	0
1	1	0	0	I	0	0	0	0	0	0
1	1	1	I	0	0	0	0	0	0	0