



---

# **DLD Lab-06**

## **Subtractor**

---



**Instructor: Mazhar Iqbal**

**EL227 – Digital Logic Design-Lab**

**SEMESTER SPRING 2023**

## Contents

1. Objectives: .....	2
2. Equipment Required: .....	2
3. What is Subtractor ? .....	2
4. Half subtractor .....	2
5. FULL Subtractor.....	3
6. K-Map Minimization .....	4
7. Applications .....	5

## 1. Objectives:

To become familiar with the operation of adders and Subtractors

## 2. Equipment Required:

- DEV-2765E Trainer Board/ Multisim 14.2 /Logic.ly
- 7486 quad 2-input XOR gate IC
- 7404 Hex Inverter gate IC
- 7408 quad 2-input AND gate IC
- 7432 quad 2-input OR gate IC

## 3. What is Subtractor ?

Subtractor is an electronic logic circuit for calculating the difference between two binary numbers which provides the difference and borrow as output.


## 4. Half subtractor

Half Subtractor is used for subtracting one single bit binary number from another single bit binary number. It has two inputs; Minuend (A) and Subtrahend (B) and two outputs; Difference (D) and Borrow (B<sub>out</sub>).

### □ Truth Table


Input		Output	
A	B	Difference (D)	Borrow (B <sub>out</sub> )
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

For D:

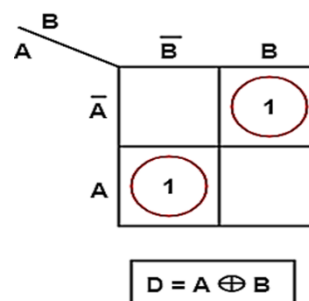

$$\text{Difference} = A \oplus B$$

For b:

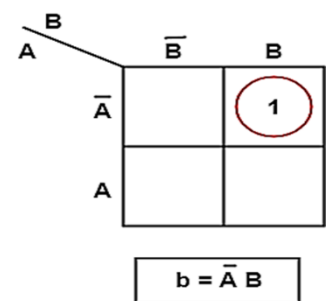


$$\text{Difference} = A \oplus B$$

From the truth table and K-map, the Boolean Expression can be derived as:

$$\text{Difference (D)} = A'.B + A.B'$$

$$A'.B + A.B' = A \oplus B$$
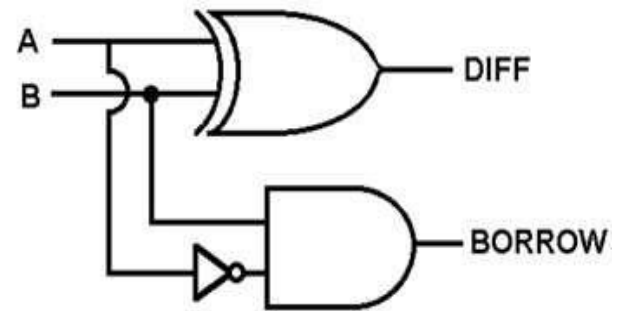
$$\text{Borrow (B}_{\text{out}}) = \bar{A}.B$$



## 5. FULL Subtractor

A logic Circuit Which is used for subtracting three single bit binary numbers is known as Full Subtractor.

It has three inputs; Minuend (A), Subtrahend

(B) and following Subtrahend (C) and two outputs; Difference (D) and Borrow ( $B_{\text{out}}$ ).

### ❑ Truth Table

Input			Output	
A	B	B(in)	D	$B_{\text{(out)}}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

## □ Solving Truth Table using K-Map

For D:

		$B B_{in}$			
$A$	$\bar{A}$	$\bar{B} \bar{B}_{in}$	$\bar{B} B_{in}$	$B B_{in}$	$B \bar{B}_{in}$
	$A$	$\bar{B} \bar{B}_{in}$	$\bar{B} B_{in}$	$B B_{in}$	$B \bar{B}_{in}$
	$\bar{A}$		1		1
	$A$	1		1	

$$D = A \oplus B \oplus B_{in}$$

For  $B_{in}$ :

		$B B_{in}$			
$A$	$\bar{A}$	$\bar{B} \bar{B}_{in}$	$\bar{B} B_{in}$	$B B_{in}$	$B \bar{B}_{in}$
	$A$	$\bar{B} \bar{B}_{in}$	$\bar{B} B_{in}$	$B B_{in}$	$B \bar{B}_{in}$
	$\bar{A}$		1	1	1
	$A$			1	

$$B_{out} = \bar{A} B + (\bar{A} + B) B_{in}$$

## 6. K-Map Minimization

From the Truth Table The Difference and Borrow will written as,

$$\text{Difference} = A'B'C + A'BC' + AB'C' + ABC$$

$$\text{Reducing it we got, Difference} = A \oplus B \oplus C$$

$$\text{Borrow} = A'B'C + A'BC' + A'BC + ABC$$


$$= A'B'C + A'BC' + A'BC + A'BC + A'BC + ABC$$

$$=A'C(B'+B)+A'B(C'+C)+BC(A'+A) \text{ Borrow}=A'C+A'B+BC$$

From the truth table and k-map minimization, the Boolean Expression can be derived as:

$$\mathbf{D} = \mathbf{A} \oplus \mathbf{B} \oplus \mathbf{C}$$
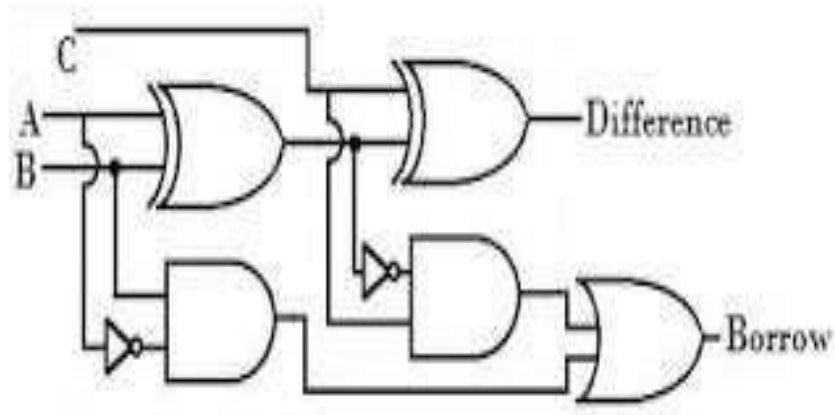
$$\mathbf{B_{(out)}} = \mathbf{BC} + (\mathbf{B} \oplus \mathbf{C}) \mathbf{A}$$



## 7. Applications

- To attenuate the radio/audio signal
- In amplifier to reduce sound distortion
- In arithmetic logic unit of processors
- Increment and decrement operators
- Calculate addresses

## 8. Lab Task

1. Design and implement the circuitry for a Half subtractor.
2. Implement a half subtractor using AND, OR and NOT gates only.
3. Implement a half subtractor using IC-74LS139.
4. Design and implement the circuitry of a full subtractor.